



ELEC1100 - Tutorial 5

Introduction to Lab Homework

❖ Weeks 7-8

- Go to your **Canvas lab page** ([LA1/LA2/LA3](#))
- Find “homework questions” & “Homework summary sheet”
- There are 3 questions in this lab homework
- Follow the given steps in “homework questions”
- Complete the “summary sheet” and **submit** to your **Canvas lab page** ([LA1/LA2/LA3](#)) before the deadline.

Submission Deadline: 11:50am (in the morning) on Apr 09 (Thu)

❑ Penalty mark on late submission

- 50% penalty mark will be given to a late submission within 3 hours.
- Zero mark will be given to more than 3-hour late submission.

❑ Submit as a single **Word document**

- Follow the scheme given in the summary sheet, type in your answers.
(or draw diagrams, or paste the screenshot of your Tinkercad simulation results)
- Pasting photos of handwritten steps are acceptable.
- It is your responsibility to ensure that the handwritten parts are readable.

Those in cursive handwriting will NOT be graded.

□ About Discussion

- It is allowed to discuss with others regarding the general approaches.
- It is **NOT acceptable** to work together on a detailed solution, to copy a solution, or give away a solution.

□ This lab homework accounts for 15% of your overall grade

Copying from each other will result in zero mark

❖ Hot Topics



- Resistance, Resistor
- Transistor
- Basic logic gates
- Truth table & K-map (you need to use what you learn in [Lecture 11 & 12](#) for Q3)

❖ Skills required

- Do simple math & deduction
- Circuit building & debugging
- Logic system design & verification

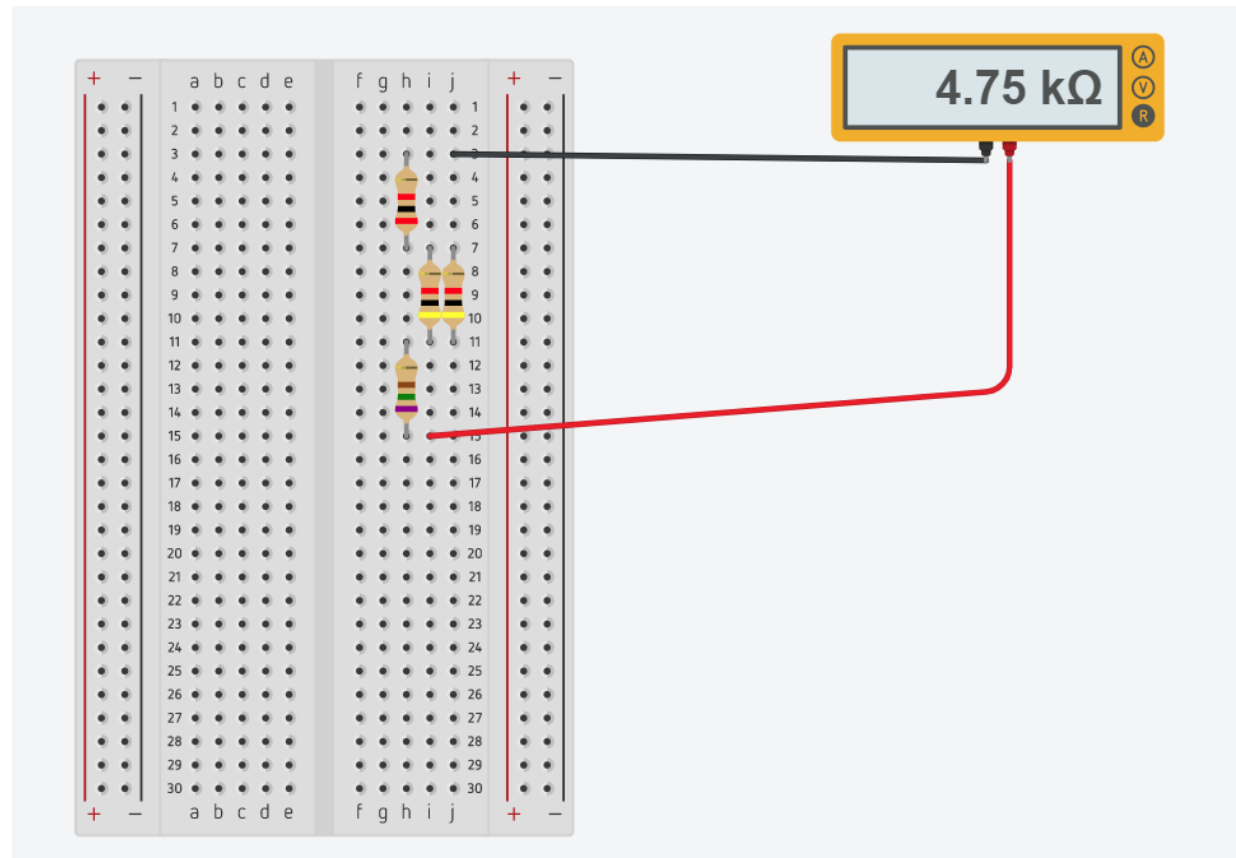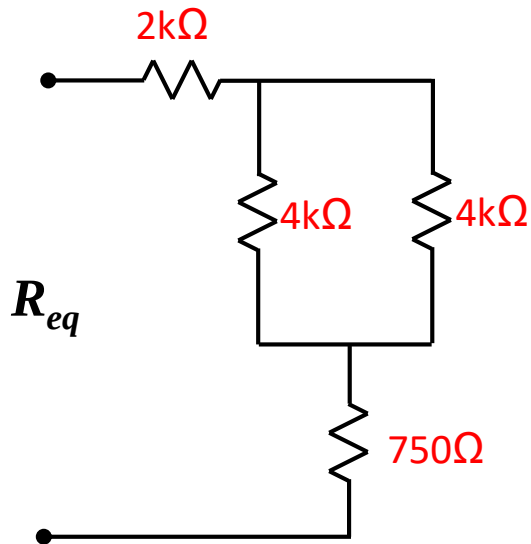
Example Question [1]

- **Measure** the equivalent resistance R_{eq} in Tinkercad



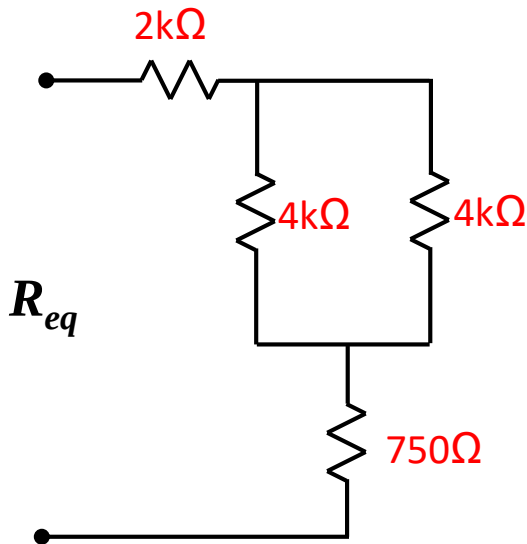Example Question [1]

- Calculate for the equivalent resistance R_{eq}




$$R_{eq} = 2k + \frac{1}{\frac{1}{4k} + \frac{1}{4k}} + 0.75k$$
$$= 4.75k$$

****The calculated R_{eq} should match with the reading on Multimeter**

Note: Use your own *student ID* number for Homework Question 1

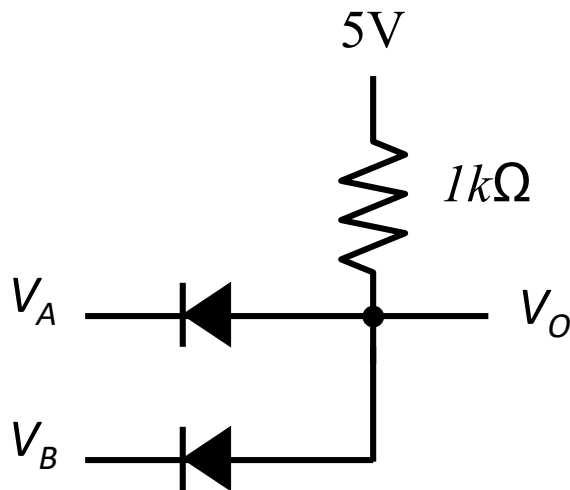
Example Question [2]

- **Construct** the circuit in Tinkercad, and measure the output voltage V_O to fill in the table with given values of V_A and V_B




V_A	V_B	V_O
0V	0V	
0V	5V	
5V	0V	
5V	5V	


Example Question [2]

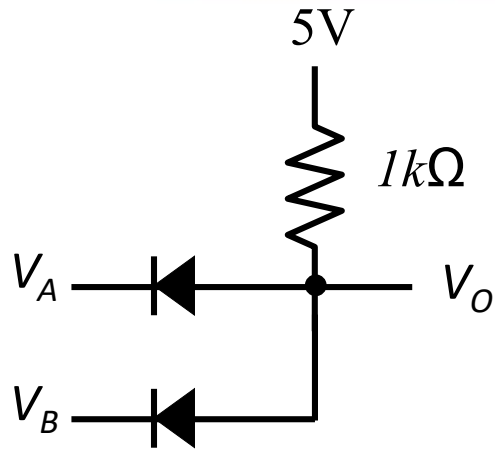


✦ $V_A = 0V$
✦ $V_B = 0V$

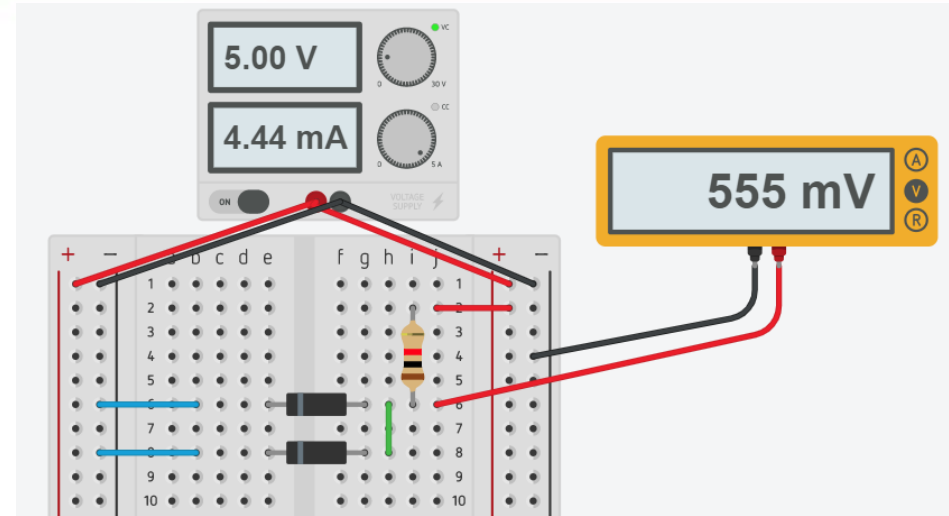


✦ $V_A = 0V$
✦ $V_B = 5V$

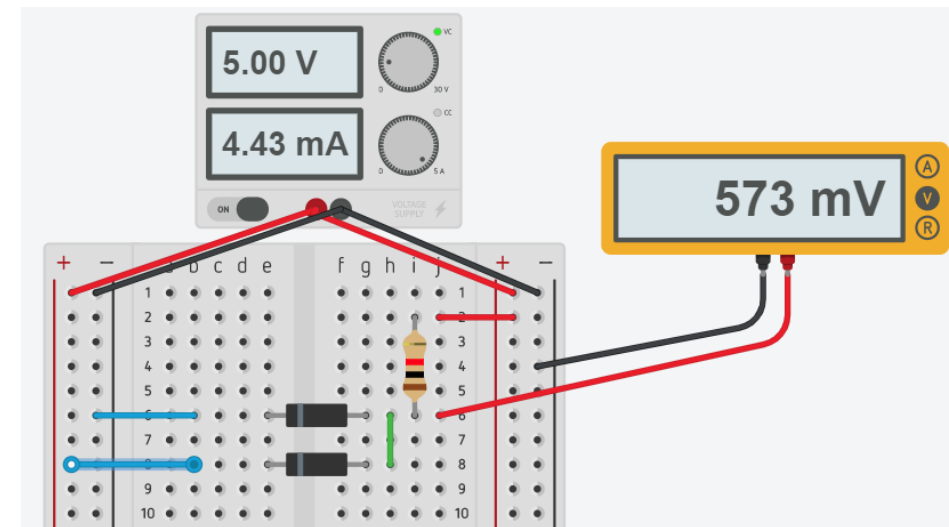


Example Question [2]

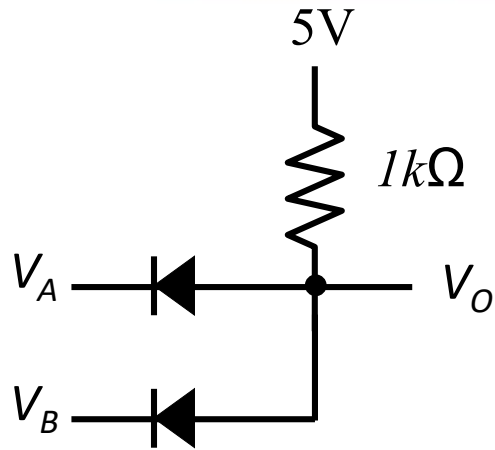


✦ $V_A = 5V$
✦ $V_B = 0V$

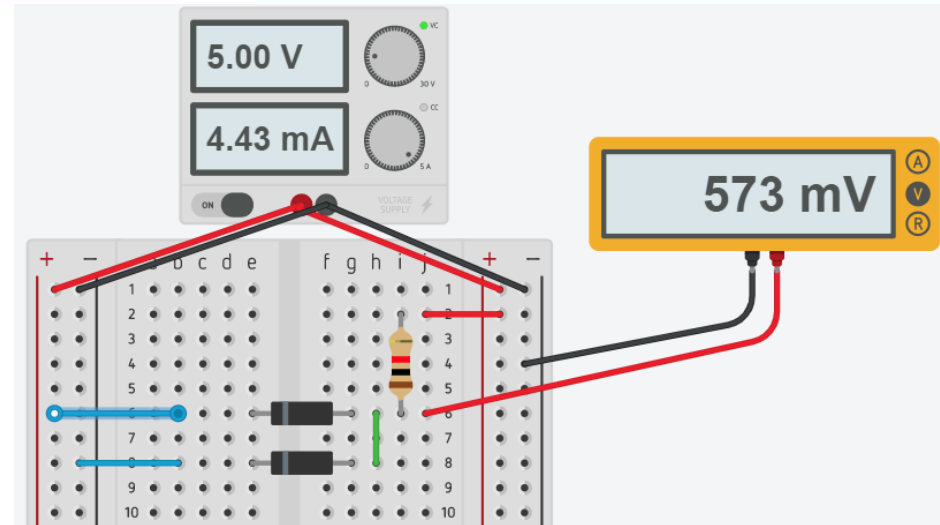

✦ $V_A = 5V$
✦ $V_B = 5V$

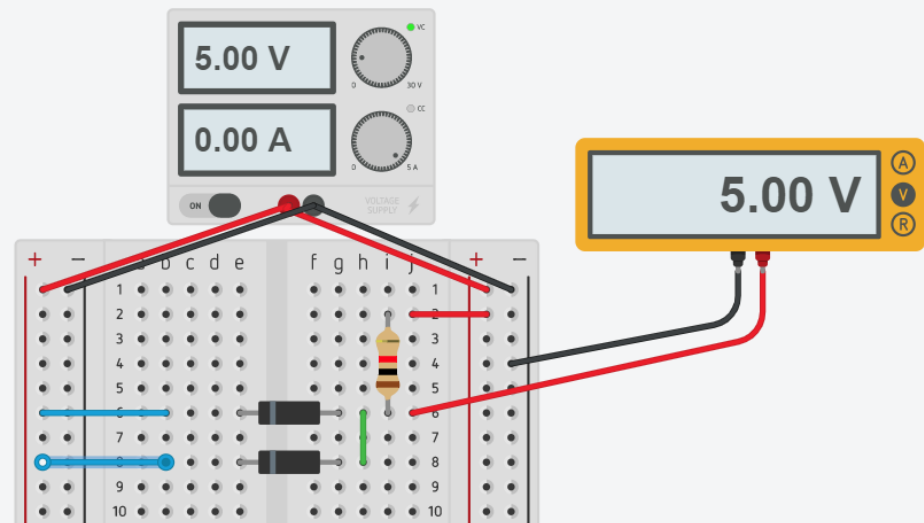

Example Question [2]

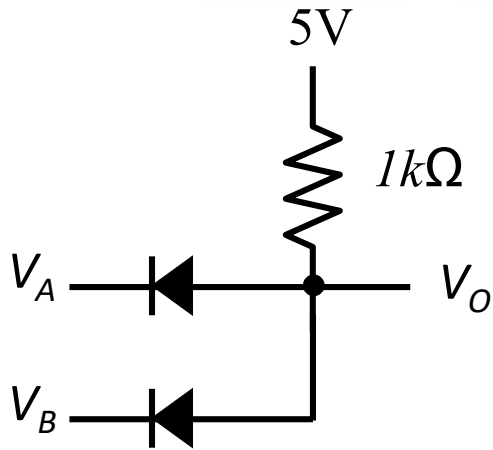


Translate the *voltages* into binary *truth table*

V_A	V_B	V_O
0V	0V	0.555V
0V	5V	0.573V
5V	0V	0.573V
5V	5V	5V

V_A	V_B	V_O
0	0	0
0	1	0
1	0	0
1	1	1

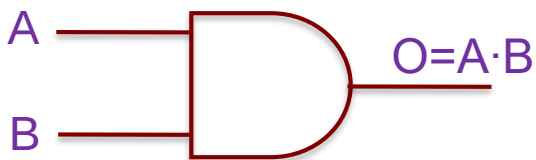Q: Which logic gate is implemented by this diodes circuit?




2-inputs AND gate

Homework Task 3




❖ Digital Dice Decoder

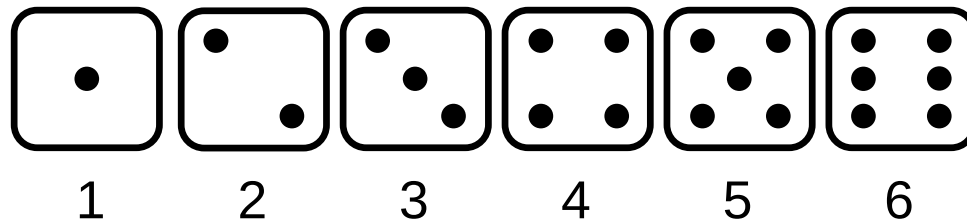- On each of its **six sides**, one of the following patterns appears, representing the numbers **1** to **6**.



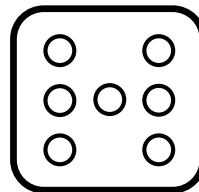
- You can think of them as seven lights to be turned “**ON**” with a given “High” voltage. By turning on the appropriate lights, you can create any one of the six patterns on the face of a dice.




Homework Task 3

❖ Digital Dice Decoder

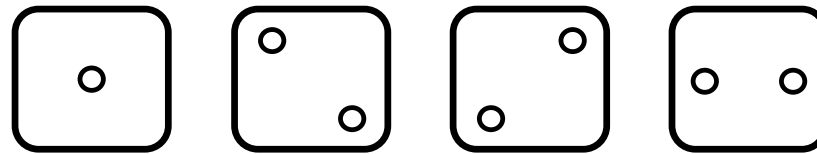- On closer inspection, there are only **four unique patterns** from which the pattern for any face can be formed.



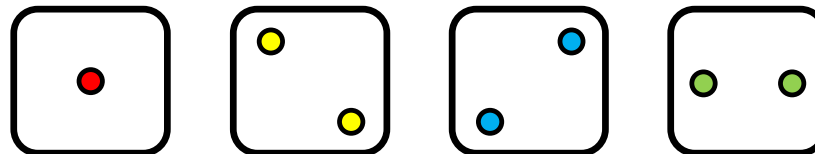- If we use *different colors* for each of these base patterns, a digital dice display can be made using 4 sets of LEDs: “Red”, “Yellow”, “Blue”, “Green”.



Homework Task 3


Given by 3 bit
binary input
B2, B1, B0.

Dice face	B2	B1	B0	Four Base Patterns			
				Red	Yellow	Blue	Green
	0	0	0				
1	0	0	1	✓			
2	0	1	0		✓		
3	0	1	1	✓	✓		
4	1	0	0		✓	✓	
5	1	0	1	✓	✓	✓	
6	1	1	0		✓	✓	✓
	1	1	1				

Homework Task 3

❖ Task

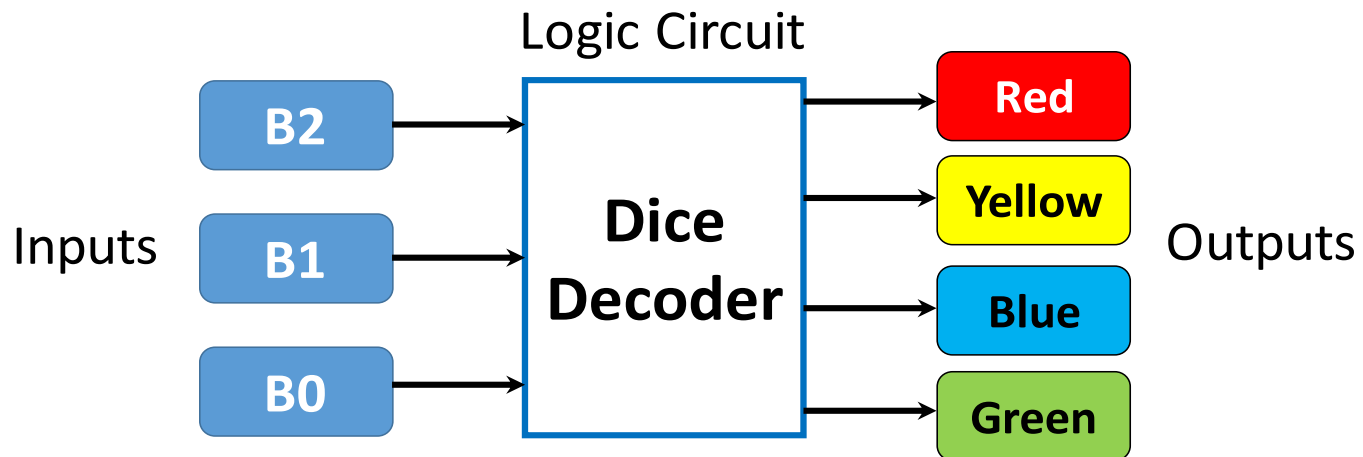- Design a logic circuit to control the **four base patterns** (Red, Yellow, Blue and Green) displaying the dice face according to the binary input **B2, B1, B0** indicating numbers **1 to 6**.



Homework Task 3

In this Tutorial, we will show the design steps of “Red” pattern as an given example

Step 1: complete the truth table

B2	B1	B0	“Red”
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Step 2: Draw K-map

	B2'B1' 00	B2'B1 01	B2B1 11	B2B1' 10
B0' 0	0	0	0	0
B0 1	1	1	0	1


Step 3: Find the logic expression

$$\text{“Red”} = B2'B0 + B1'B0$$

Homework Task 3

Step 4: Draw logic gates implementation diagram

Logic Gates

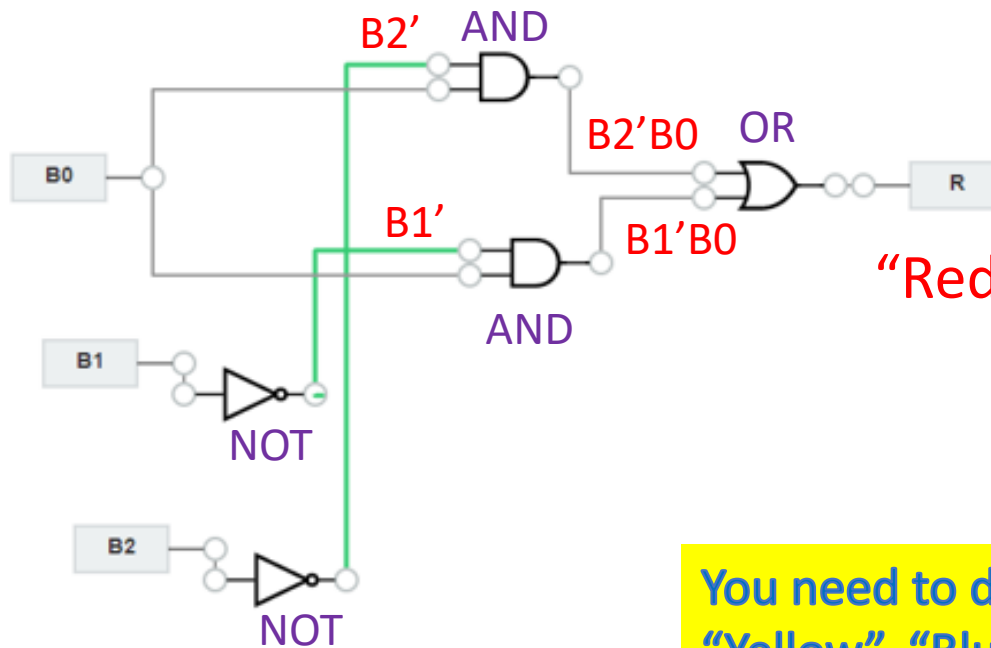

$$\text{"Red"} = B2'B0 + B1'B0$$

You need to design for obtaining "Yellow", "Blue", "Green" patterns logic implementation diagrams as well.



Homework Task 3

Step 5: Construct the logic implementation circuit in **Tinkercad**

Note:

- ❖ You need to obtain all of the logic diagrams for the four light patterns first, then start working in Tinkercad
- ❖ It's recommended to count for how many NOT/AND/OR gates you need to use, *plan your circuit layout*, in order to optimize your breadboard arrangement

Homework Task 3

❖ Logic Gate: NOT

NOT: One input, one output



- Output is the “inversion” of input
- i.e. If input is 5V, then output is 0V

Input	Output
0	1
1	0

NOT Gates in Tinkercad



6 NOT gates on one IC

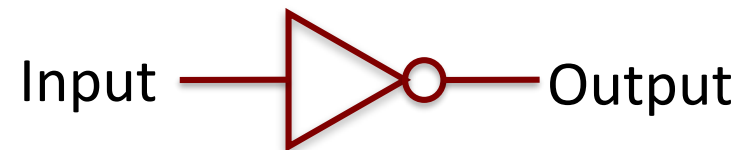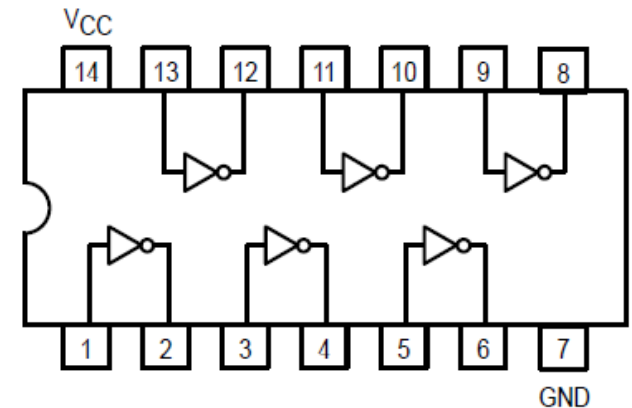

Homework Task 3

❖ Logic Gate: AND

AND: Two inputs, one output



- Output is high only when both inputs are high

Input 1	Input 2	Output
0	0	0
0	1	0
1	0	0
1	1	1

AND Gates in Tinkercad



4 AND gates on one IC

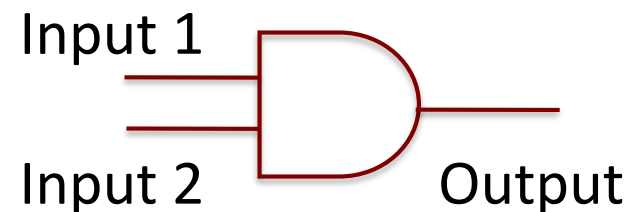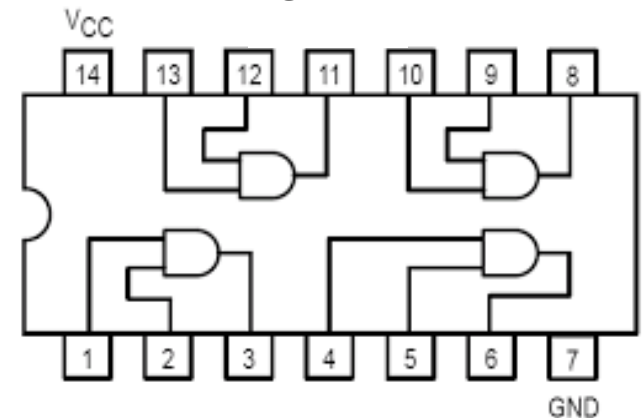

Homework Task 3

❖ Logic Gate: OR

OR: Two inputs, one output



- Output is low only when both inputs are low

Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	1

OR Gates in Tinkercad



4 OR gates on one IC

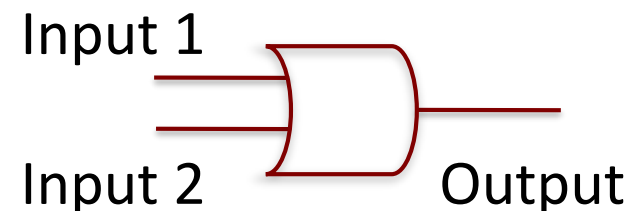
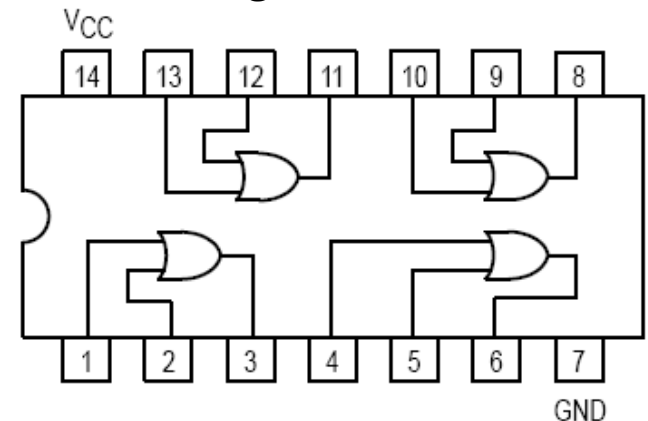


Homework Task 3

❖ 3-Input AND Gate




3 gates on one IC

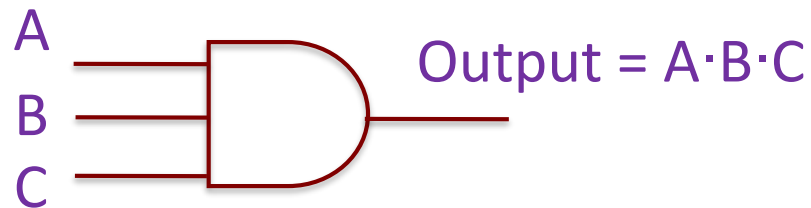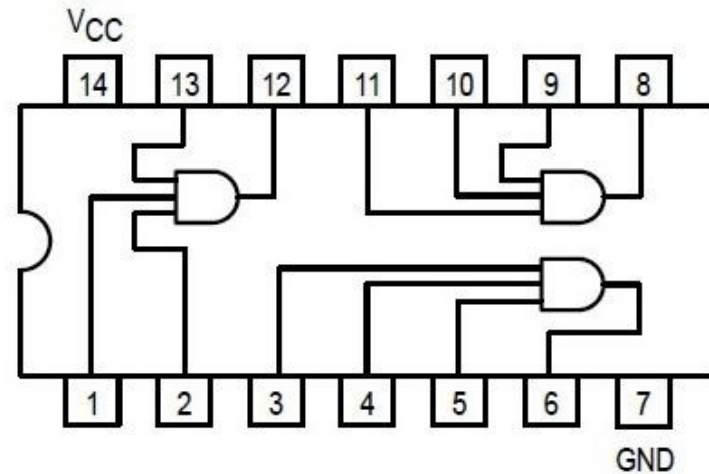


Homework Task 3

❖ Arrange your LED lights as below

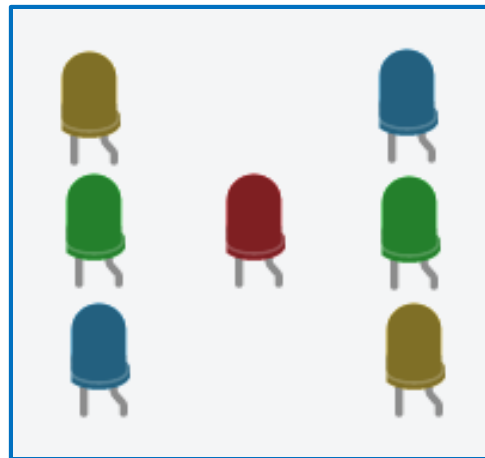

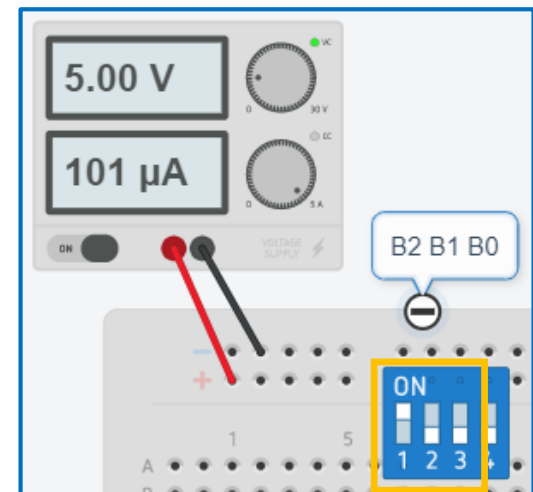****add 1k Ω resistor for protection!!!**

❖ DIP Switch to easily change the input B2B1B0



Homework Task 3

❖ Q17 in Task 3: Use your own SID number

Display Dice Face of number “**y**”, where $y = \text{mod}(x, 6) + 1$

Let **x** be the last digit of your student ID.

Your student ID: 1234567**8**

Your Dice Face number “**y**” = $\text{mod}(8, 6) + 1 = 3$

Your binary input: B2B1B0=011

Dice face	B2 B1 B0		Four Base Patterns			
			Red	Yellow	Blue	Green
3	0 1 1		✓	✓		